

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

FIRST SEMESTER M.TECH DEGREE EXAMINATION, DECEMBER 2015

**Electronics & Communication Engineering****( COMMUNICATION ENGINEERING & SIGNAL PROCESSING)****07EC6249 RF System Design**

Max. Marks : 60

Duration: 3 Hours

Answer all six questions. Part 'a' of each question is compulsory.

Answer either part 'b' or part 'c' of each question

**MODULE I**

1. (a) Define characteristic Impedance of a transmission line ? Derive an equation for characteristic impedance related with the primary constants of the transmission line ?

**4 Marks****Answer b or c**

- (b) What is a lossless transmission line ? Show that the impedance of a lossless transmission line at maximum voltage or minimum current is  $Z(l) = Z_0 \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$

**5 Marks**

- (c) The VSWR of a lossless,  $75\Omega$  transmission line is 4. Calculate the impedance at the voltage maximum and minimum in the standing wave pattern along the line.

**5 Marks****MODULE II**

2. (a) Explain the steps to find VSWR using Smith chart ?

**4 Marks****Answer b or c**

- (b) Show that in a smith chart the constant reactance circles is given by the equation  $(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$  which represents a group of circles with center  $\left(1, \frac{1}{x}\right)$  and radius  $\frac{1}{x}$


**5 Marks**

- (c) Consider the following transmission line of length  $l$  with characteristic impedance  $Z_0$  connected to a load impedance  $Z_L$ .  
Using smith chart describe how to find the following :
- (i) The SWR on the line
  - (ii) The reflection coefficient at the load
  - (iii) The load admittance
  - (iv) The input impedance of the line

**5 Marks**

### MODULE III

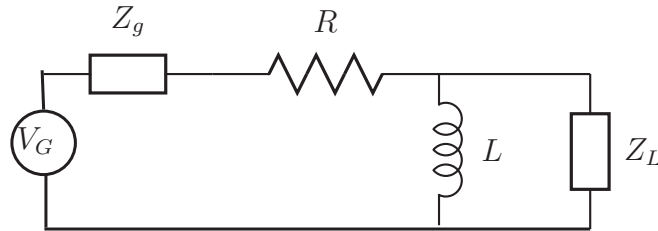3. (a) Consider the following RF High pass filter :



Find the insertion loss of the above filter


**4 Marks**

### Answer b or c

- (b) Consider an RF Filter which is obtained by cascading two two-port networks with individual scattering matrices  $[S^A]$  and  $[S^B]$ . Find the overall  $S_{21}$  parameter of the RF Filter.

**5 Marks**

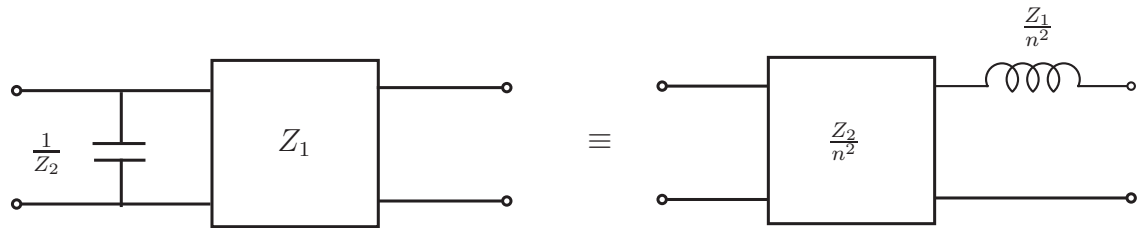- (c) Consider the Kuroda's Identity shown below :



Using ABCD parameters of two circuits show that the two circuits are identical if we choose  $n^2 = 1 + \frac{Z_2}{Z_1}$

**5 Marks**

## MODULE IV

4. (a) Explain how a single stub open circuited series matching network is designed using smith chart ?

**4 Marks**

**Answer b or c**

- (b) Show that for a single stub open circuited series matching network the length of the stub  $l_1$  from the load where the stub is to be connected is given by

$$\frac{l_1}{\lambda} = -\frac{1}{2\pi} \tan^{-1} \left( \frac{B_L}{2Y_0} \right) \text{ for } G_L = Y_0 \text{ where } Y_L = G_L + jB_L.$$

**5 Marks**

- (c) Explain how double stub short circuited shunt matching network is designed using smith chart ?

**5 Marks**

## MODULE V

5. (a) Consider a single stage RF amplifier as a two port network.

$$\text{Show that the Power Gain, } G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)}$$

**5 Marks**

**Answer b or c**

- (b) Show that the input stability circle represented in a complex  $\Gamma$  plane is of the form  $|\Gamma_S - C_S| = |R_S|$  where center  $C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$  and radius  $R_S = \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2}$  where  $\Delta = S_{11}S_{22} - S_{12}S_{21}$

**7 Marks**

- (c) Design a single section quarter wave transformer to match a  $10\Omega$  load to a  $50\Omega$  line at  $f_0 = 3$  GHz. What would be the reflection coefficient corresponding to a SWR of 1.5 ?

**7 Marks**

## MODULE VI

6. (a) Describe the basics of RF Oscillator ?

**5 Marks**

**Answer b or c**

(b) Explain a single ended Mixer ?

**7 Marks**

(c) Describe a negative resistance oscillator ? Find the conditions for steady state oscillations ?

**7 Marks**